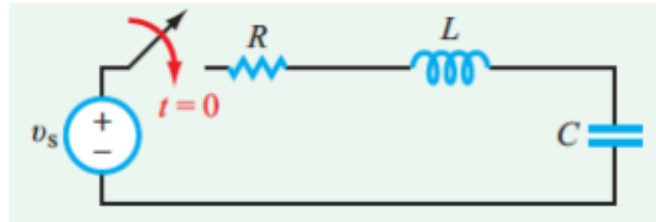


Lecture 6 Second-Order Circuits

What if we have both L and C in the circuit

Series RLC Circuits




when $i_L(0_-) = 0, v_c(0_-) = 0$ find $V_c(t)$

$$\begin{cases} i_L(t) = C \frac{dv_c(t)}{dt} \\ V_s - R \cdot i_L(t) - L \frac{di_L(t)}{dt} - v_c(t) = 0 \end{cases} \Rightarrow RC \frac{dv_c(t)}{dt} + LC \frac{d^2 v_c(t)}{dt^2} + v_c(t) = v_s$$

$$\frac{d^2 v_c(t)}{dt^2} + \frac{R}{L} \frac{dv_c(t)}{dt} + \frac{1}{LC} v_c(t) = \frac{v_s}{LC}$$


这是一个二阶方程，所以也是二阶电路。second order circuit

Initial and Final condition

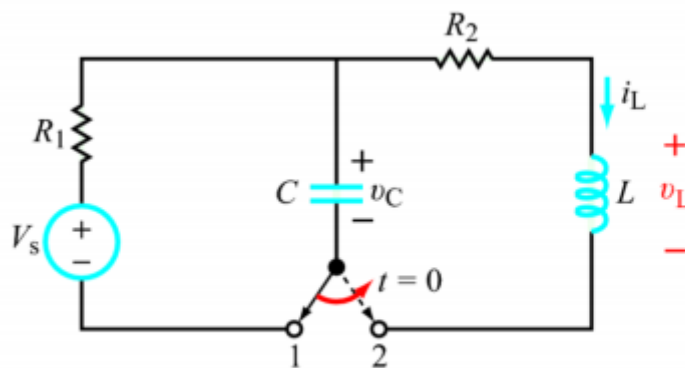

Find $v_c(0_-), i_c(0_-), i_L(0_-), v_L(0_-),$
 $v_c(0_+), i_c(0_+), i_L(0_+), v_L(0_+),$
 $v_c(\infty), i_c(\infty), i_L(\infty), v_L(\infty)$

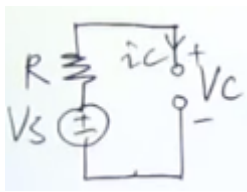1. $t = 0_-$ steady state capacitor likes open circuit inductor like short circuit




$$v_c(0_-) = v_s$$

$$i_c(0_-) = 0$$

$$i_L(0_-) = 0$$

$$v_L(0_-) = 0$$

2. $t = 0_+$ 电容电压不突变，电感电流不突变

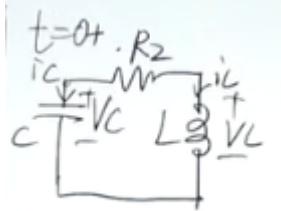

$$v_c(0_+) = v_s$$

$$i_c(0_+) = 0$$

$$i_L(0_+) = 0$$

$$v_L(0_+) = v_s$$

3. $t = \infty$

$$v_c(\infty) = 0$$

$$i_c(\infty) = 0$$


$$i_L(\infty) = 0$$

$$v_L(\infty) = 0$$

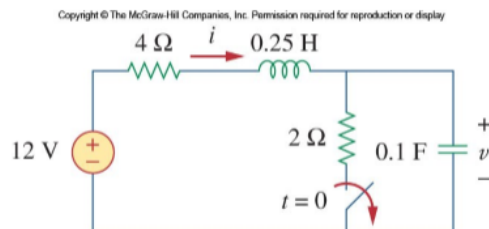
Example

- The switch has been closed for a long time. It is open at $t = 0$. Find

- $i(0_+)$, $v(0_+)$
- $di(0_+)/dt$, $dv(0_+)/dt$
- $i(\infty)$, $v(\infty)$



1. $t = 0_-$

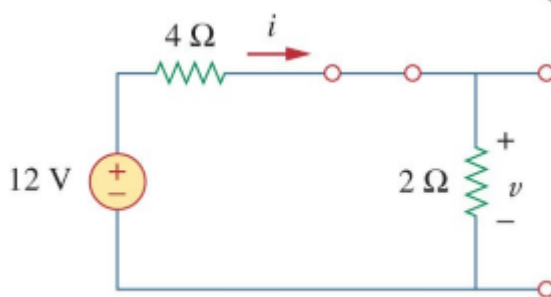


$$i(0_-) = 12/6 = 2A$$

$$v(0_-) = 2 \cdot 2 = 4V$$

(a)


2. $t = 0_+$

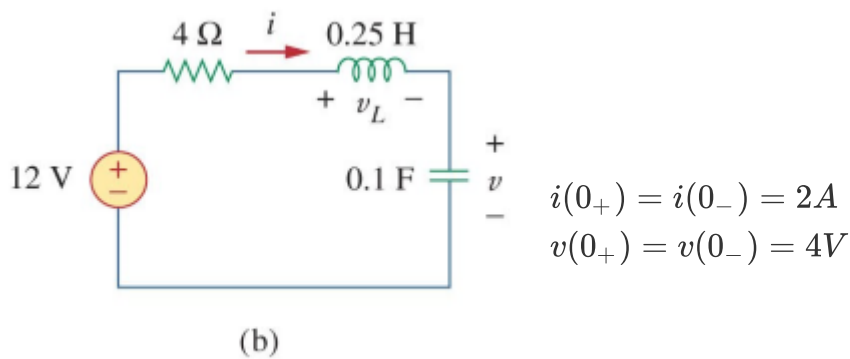

$$\frac{di(0_+)}{dt} = \frac{1}{L} V_L(0_+) = 12 - 2 * 4 - 4 = 0A/s$$


$$\frac{dv(0_+)}{dt} = \frac{1}{C} i_C(0_+) = 2/0.1 = 20V/s$$

3. $t = \infty$

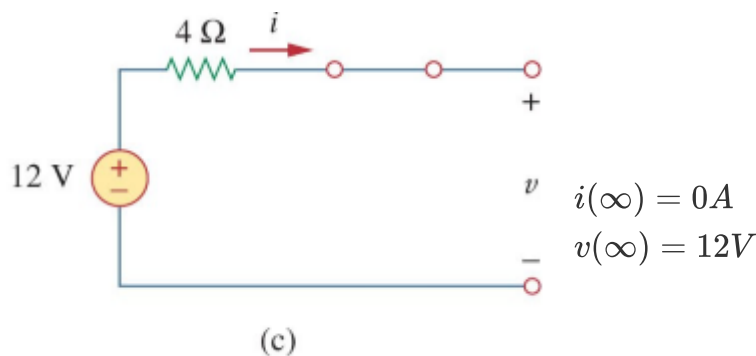

Natural Response自然响应，零输入响应

series RLC circuit

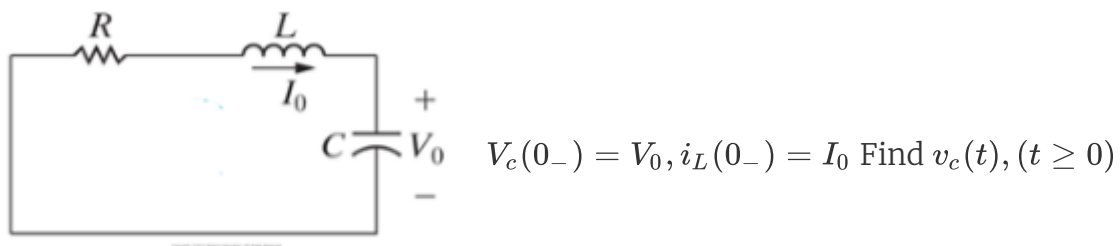

$$\begin{cases} i_L(t) = C \frac{dv_c(t)}{dt} \\ -R \cdot i_L(t) - L \frac{di_L(t)}{dt} - v_c(t) = 0 \end{cases} \Rightarrow RC \frac{dv_c(t)}{dt} + LC \frac{d^2 v_c(t)}{dt^2} + v_c(t) = 0$$

$$\frac{d^2 v_c(t)}{dt^2} + p \frac{dv_c(t)}{dt} + q v_c(t) = 0, \text{ where } p = \frac{R}{L}, q = \frac{1}{LC}$$

解上述二阶常系数微分方程 (2^{nd} order ordinary differential equation/ODE) 就可以解除这个电路。

Let $V_C(t) = Ae^{st}$, then $Ae^{st}(s^2 + ps + q) = 0$. Solve equation $s^2 + ps + q = 0$ about s

$$s = \frac{-p \pm \sqrt{p^2 - 4q}}{2} = \frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

So we have 3 cases here:

1. **overdamped** 过阻尼 s have two different real solution

where $\left(\frac{R}{2L}\right)^2 - \frac{1}{LC} > 0$, let $\alpha = \frac{R}{2L}$, $\omega_0 = \frac{1}{\sqrt{LC}}$ so the equation about the circuit can be interpret into $s^2 + 2\alpha s + \omega_0^2 = 0$, so that

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}.$$

Therefore $V_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$, where A_1, A_2 can be found using two initial conditions.

2. **critically damped** 临界阻尼 s have only one real solution

where $\left(\frac{R}{2L}\right)^2 - \frac{1}{LC} = 0$, let $\alpha = \frac{R}{2L}$, $\omega_0 = \frac{1}{\sqrt{LC}}$, $\alpha = \omega_0$ $s = s_1 = s_2 = -\alpha$

Therefore $V_C(t) = (A_1 t + A_2) e^{st}$, where A_1, A_2 can be found using two initial conditions.

3. **underdamped** 欠阻尼 s_1, s_2 are complex

where $\left(\frac{R}{2L}\right)^2 - \frac{1}{LC} < 0$, let $\alpha = \frac{R}{2L}$, $\omega_0 = \frac{1}{\sqrt{LC}}$ so the equation about the circuit can be interpret into $s^2 + 2\alpha s + \omega_0^2 = 0$, so that

$$s_{1,2} = -\alpha \pm \sqrt{\omega_0^2 - \alpha^2} i, \text{ seeing that } V_C(t) \in \mathbb{R}$$

$$\begin{aligned} c_1 e^{s_1 t} + c_2 e^{s_2 t} &= c_1 e^{-(\alpha + j\omega_d i)t} + c_2 e^{-(\alpha - j\omega_d i)t} \\ (c_1 e^{s_1 t} + c_2 e^{s_2 t})^* &= c_1^* e^{-(\alpha - j\omega_d i)t} + c_2^* e^{-(\alpha + j\omega_d i)t} \end{aligned}$$


so that $c_1 = c_2^*$, then

$$v_c(t) = e^{-\alpha t} [A_1 \cos \omega_d t + A_2 \sin \omega_d t]$$

Summary series RLC network


Case		$\alpha = \frac{R}{2L}, \omega_0 = \sqrt{\frac{1}{LC}}$	
1	overdamped	$\alpha > \omega \Leftrightarrow R > 2\sqrt{\frac{L}{C}}$	$V_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$
2	critically damped	$\alpha = \omega \Leftrightarrow R = 2\sqrt{\frac{L}{C}}$	$V_C(t) = (A_1 t + A_2) e^{st}$ $s = -\alpha$
3	underdamped	$\alpha < \omega \Leftrightarrow R < 2\sqrt{\frac{L}{C}}$	$V_C(t) = e^{-\alpha t} [A_1 \cos \omega_d t + A_2 \sin \omega_d t]$ $\omega_0 = \sqrt{\omega_0^2 - \alpha^2}$

Image

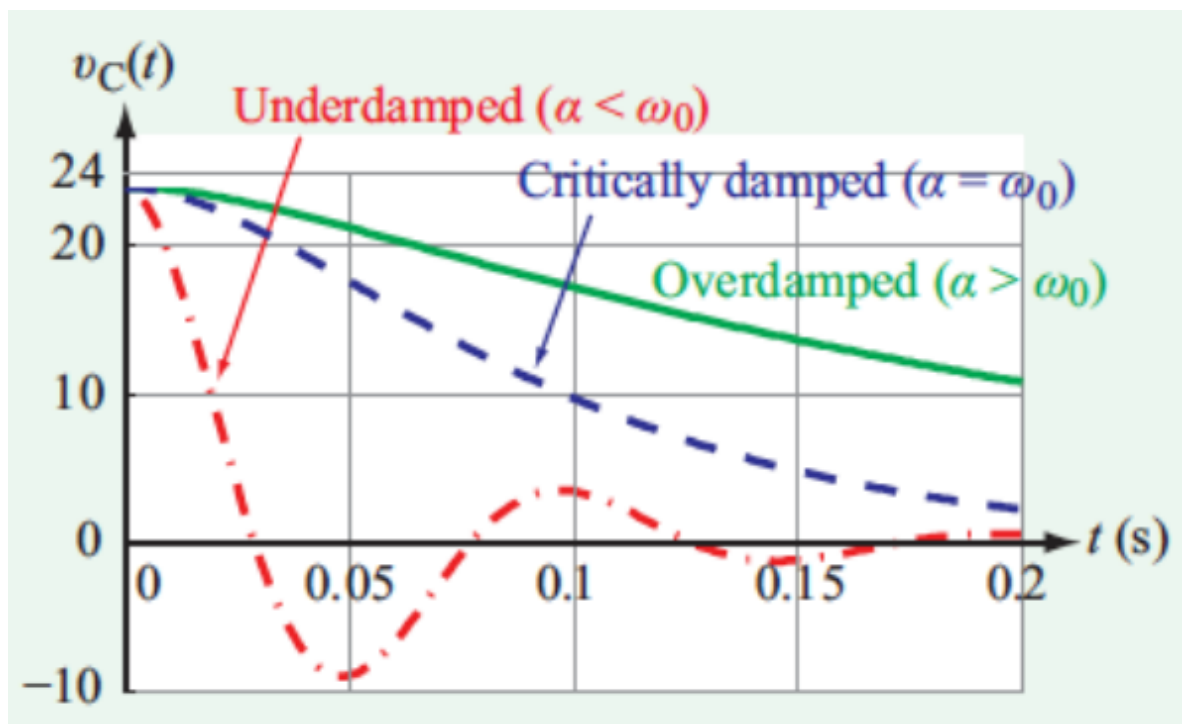


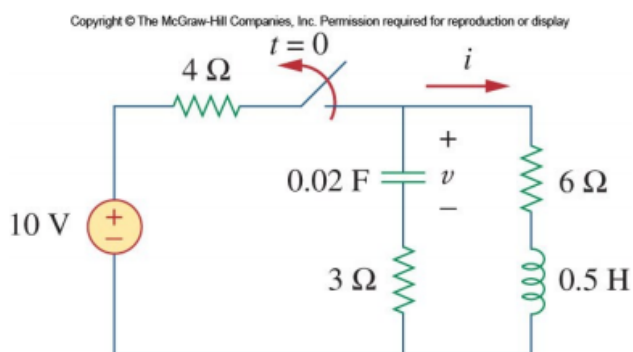
Example

Find $v(t)$ & $i(t)$ in the circuit below. Assume the circuit has reached steady state at $t = 0^-$.



$$\alpha = \frac{R}{2L} = 9 \quad \omega_0 = \frac{1}{\sqrt{LC}} = 10$$
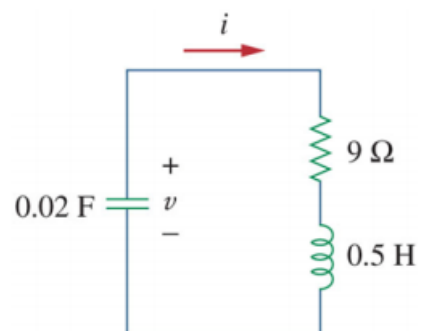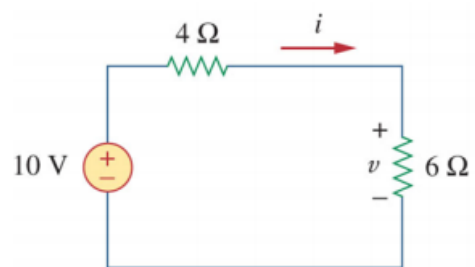
$$s_{1,2} = -\alpha \mp \sqrt{\alpha^2 - \omega_0^2} = -9 \mp j4.359$$



Handwritten solution for $v(t)$:

$$v(t) = e^{-\alpha t} [A_1 \cos \omega_d t + A_2 \sin \omega_d t]$$

$$= e^{-9t} [A_1 \cos 4.359t + A_2 \sin 4.359t]$$

From $i(0_+) = 1A$

$$\Rightarrow -C \frac{dV(0_+)}{dt} = 1A \Rightarrow \frac{dV(0_+)}{dt} = -50V/s.$$


$$\Rightarrow \begin{cases} \frac{dV(0_+)}{dt} = -9A_1 + 4.359A_2 = -50 \\ V(0_+) = A_1 = 6 \end{cases} \Rightarrow \begin{cases} A_1 = 6 \\ A_2 = 0.918 \end{cases}$$

$$\Rightarrow v(t) = e^{-9t} (6 \cos 4.359t + 0.918 \sin 4.359t) V$$

More Notes

Case		$\alpha = \frac{R}{2L}, \omega_0 = \sqrt{\frac{1}{LC}}$	
1	overdamped	$\alpha > \omega \Leftrightarrow R > 2\sqrt{\frac{L}{C}}$	$V_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$ $\begin{cases} s_1 A_1 + s_2 A_2 = \frac{i(0_+)}{C} \\ A_1 + A_2 = v(0_+) \end{cases}$
2	critically damped	$\alpha = \omega \Leftrightarrow R = 2\sqrt{\frac{L}{C}}$	$V_C(t) = (A_1 t + A_2) e^{st}$ $s = -\alpha$ $\begin{cases} A_1 + s A_2 = \frac{i(0_+)}{C} \\ A_2 = v(0_+) \end{cases}$
3	underdamped	$\alpha < \omega \Leftrightarrow R < 2\sqrt{\frac{L}{C}}$	$V_C(t) = e^{-\alpha t} [A_1 \cos \omega_d t + A_2 \sin \omega_d t]$ $\omega_0 = \sqrt{\omega_0^2 - \alpha^2}$ $\begin{cases} \omega_0 A_2 - \alpha A_1 = \frac{i(0_+)}{C} \\ A_1 = v(0_+) \end{cases}$

parallel RLC circuit

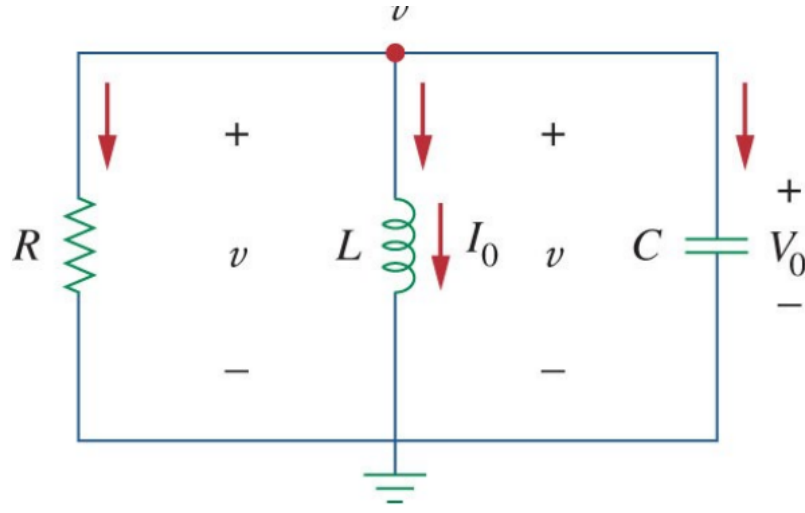

$$\begin{cases} V_c(t) = L \frac{di_L(t)}{dt} \\ \frac{V_c}{R} + i_L + C \frac{dV_c}{dt} = 0 \end{cases} \Rightarrow \frac{L}{R} \frac{di_L(t)}{dt} + LC \frac{d^2 i_L(t)}{dt^2} + i_L(t) = 0$$

$$\Rightarrow \frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = 0$$

1. **overdamped** 过阻尼 s have two different real solution

where $(\frac{1}{2RC})^2 - \frac{1}{LC} > 0$, let $\alpha = \frac{1}{2RC}$, $\omega_0 = \frac{1}{\sqrt{LC}}$ so the equation about the circuit can be interpret into $s^2 + 2\alpha s + \omega_0^2 = 0$, so that

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}.$$

Therefore $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$, where A_1, A_2 can be found using two initial conditions.

2. **critically damped** 临界阻尼 s have only one real solution

where $(\frac{1}{2RC})^2 - \frac{1}{LC} = 0$, let $\alpha = \frac{1}{2RC}$, $\omega_0 = \frac{1}{\sqrt{LC}}$, $\alpha = \omega_0$ $s = s_1 = s_2 = -\alpha$

Therefore $i_L(t) = (A_1 t + A_2) e^{st}$, where A_1, A_2 can be found using two initial conditions.

3. **underdamped** 欠阻尼 s_1, s_2 are complex

where $(\frac{1}{2RC})^2 - \frac{1}{LC} < 0$, let $\alpha = \frac{1}{2RC}$, $\omega_0 = \frac{1}{\sqrt{LC}}$ so the equation about the circuit can be interpret into $s^2 + 2\alpha s + \omega_0^2 = 0$, so that

$$s_{1,2} = -\alpha \pm \sqrt{\omega_0^2 - \alpha^2} i, \text{ seeing that } V_C(t) \in \mathbb{R}$$

$$\begin{aligned} c_1 e^{s_1 t} + c_2 e^{s_2 t} &= c_1 e^{-(\alpha + j\omega_d i)t} + c_2 e^{-(\alpha - j\omega_d i)t} \\ (c_1 e^{s_1 t} + c_2 e^{s_2 t})^* &= c_1^* e^{-(\alpha - j\omega_d i)t} + c_2^* e^{-(\alpha + j\omega_d i)t} \end{aligned}$$

so that $c_1 = c_2^*$, then

$$i_L(t) = e^{-\alpha t} [A_1 \cos \omega_d t + A_2 \sin \omega_d t]$$


Case

$$\alpha = \frac{1}{2RC}, \omega_0 = \sqrt{\frac{1}{LC}}$$

Case		$\alpha = \frac{1}{2RC}, \omega_0 = \sqrt{\frac{1}{LC}}$	
1	overdamped	$\alpha > \omega \Leftrightarrow \frac{1}{R} > 2\sqrt{\frac{L}{C}}$	$V_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$ $\begin{cases} s_1 A_1 + s_2 A_2 = \frac{i(0_+)}{c} \\ A_1 + A_2 = v(0_+) \end{cases}$
2	critically damped	$\alpha = \omega \Leftrightarrow \frac{1}{R} = 2\sqrt{\frac{L}{C}}$	$V_C(t) = (A_1 t + A_2) e^{st}$ $s = -\alpha$ $\begin{cases} A_1 + s A_2 = \frac{i(0_+)}{c} \\ A_2 = v(0_+) \end{cases}$
3	underdamped	$\alpha < \omega \Leftrightarrow \frac{1}{R} < 2\sqrt{\frac{L}{C}}$	$V_C(t) = e^{-\alpha t} [A_1 \cos \omega_d t + A_2 \sin \omega_d t]$ $\omega_0 = \sqrt{\omega_0^2 - \alpha^2}$ $\begin{cases} \omega_0 A_2 - \alpha A_1 = \frac{i(0_+)}{c} \\ A_1 = v(0_+) \end{cases}$

Step response 阶跃响应

series RLC circuit

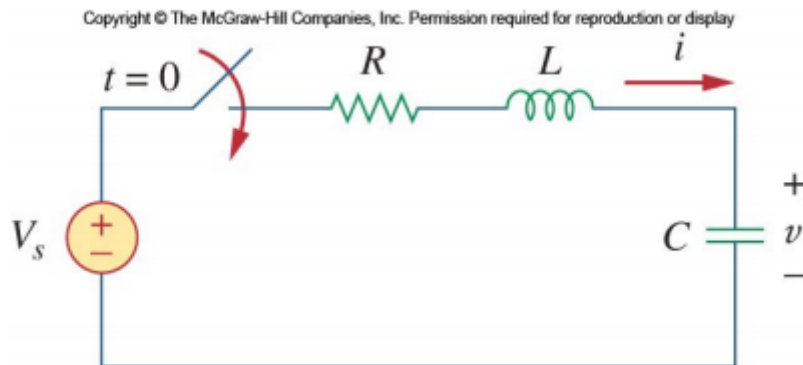

$$\frac{d^2 V}{dt^2} + \frac{R}{L} \frac{dV}{dt} + \frac{V}{LC} = \frac{V_s}{LC} \quad (*)$$

$$\text{Solution : } V(t) = \underbrace{V_t(t)}_{\text{transient response}} + \underbrace{V_{ss}(t)}_{\text{steady state response}}$$

Statement: specifically, for step response, $V_t(t)$ is the same format as in natural response, $V_{ss} = V_s$, $v(t)$ is the solution to equation(*)

Case	$\alpha = \frac{R}{2L}, \omega_0 = \sqrt{\frac{1}{LC}}$
------	---


Case		$\alpha = \frac{R}{2L}, \omega_0 = \sqrt{\frac{1}{LC}}$	
1	overdamped	$\alpha > \omega \Leftrightarrow R > 2\sqrt{\frac{L}{C}}$	$V_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + V_s$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$
2	critically damped	$\alpha = \omega \Leftrightarrow R = 2\sqrt{\frac{L}{C}}$	$V_C(t) = (A_1 t + A_2) e^{st} + V_s$ $s = -\alpha$
3	underdamped	$\alpha < \omega \Leftrightarrow R < 2\sqrt{\frac{L}{C}}$	$V_C(t) = e^{-\alpha t} [A_1 \cos \omega_d t + A_2 \sin \omega_d t] + V_s$ $\omega_0 = \sqrt{\omega_0^2 - \alpha^2}$

example

- Find $v(t)$ and $i(t)$ for $t > 0$.

Consider three cases:

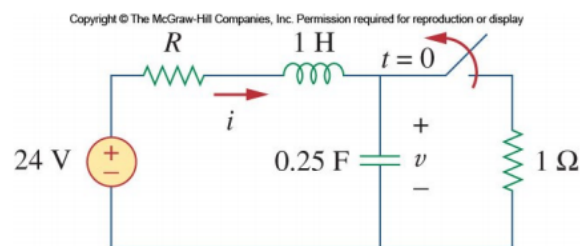- $R = 5\Omega$
- $R = 4\Omega$
- $R = 1\Omega$



When $R = 5\Omega$,

- For $t < 0$, switch closed, capacitor open, inductor shorted.


$$i(0) = 4A = C \frac{dv(0)}{dt}, \quad v(0) = 4V, \quad \frac{dv(0)}{dt} = 16$$

- For $t > 0$, switch open, a series RLC network

$$\alpha = \frac{R}{2L} = 2.5, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2, \quad s_{1,2} = -1, -4 \quad \text{Overdamped.}$$

$$v(t) = v_{ss} + (A_1 e^{-t} + A_2 e^{-4t})$$

$\alpha = \frac{5\Omega}{2 \times 1H} = 2.5 \text{ rad/s}, \quad \omega_0 = \frac{1}{\sqrt{1 \times 0.25}} \text{ rad/s} = 2 \text{ rad/s}. \quad \alpha > \omega_0.$
 overdamped.
 $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -2.5 \pm \sqrt{2.5^2 - 2^2} = -1, -4.$
 $V(t) = A_1 e^{-t} + A_2 e^{-4t} + 24V.$
 From initial conditions:
 $V(0+) = A_1 + A_2 + 24 = 4 \Rightarrow A_1 + A_2 = -20,$
 $i(0+) = C \frac{dV(t)}{dt} \Big|_{t=0+} = C(-A_1 - 4A_2) = \frac{1}{4} A_1 + A_2 = 4 \Rightarrow$
 $A_1 = -\frac{64}{3}, \quad A_2 = \frac{4}{3}. \quad V(t) = -\frac{64}{3} e^{-t} + \frac{4}{3} e^{-4t} + 24V.$

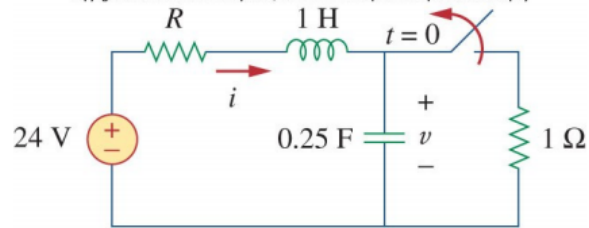

When $R = 4\Omega$,

- For $t < 0$, switch closed, capacitor open, inductor shorted.


$$i(0) = 4.8A = C \frac{dv(0)}{dt}, \quad v(0) = 4.8V, \quad \frac{dv(0)}{dt} = 19.2$$

- For $t > 0$, switch open, a series RLC network

$$\alpha = \frac{R}{2L} = 2, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2, \quad s_{1,2} = -2 \quad \text{Critically damped}$$

$$v(t) = v_{ss} + (A_1 + A_2 t)e^{-2t}$$

(b). $R=4\Omega$, $V(0^+)=4.8V$, $i(0^+)=4.8A$. Critically damped
 $\alpha = \frac{4\Omega}{2 \times 1H} = 2 \text{ rad/s}$, $\omega_0 = \frac{1}{\sqrt{1 \times 0.25}} = 2 \text{ rad/s}$. $\alpha = \omega_0$.
 $\Rightarrow S_1 = S_2 = S = -\alpha = -2$.
 $\Rightarrow V(t) = (A_1 + A_2 t)e^{-2t} + 24V$.
 $\Rightarrow V(t) = (-19.2t - 19.2)e^{-2t} + 24V$.
From Initial condition:
 $\begin{cases} V(0^+) = A_2 + 24 = 4.8 \Rightarrow A_2 = -19.2 \\ i(0^+) = C \frac{dV(t)}{dt} \Big|_{t=0^+} = C(A_1 - 2A_2) = \frac{1}{4}A_1 - \frac{1}{2}A_2 = 4.8 \end{cases} \Rightarrow A_1 = -19.2$

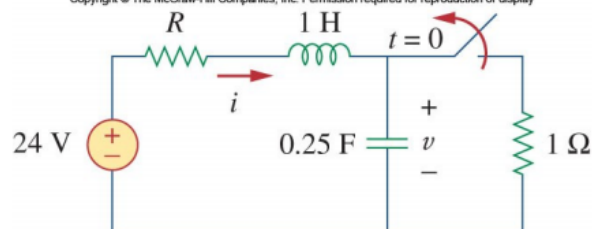

When $R = 1\Omega$,

- For $t < 0$, switch closed, capacitor open, inductor shorted.

$$i(0) = 12A = C \frac{dv(0)}{dt}, \quad v(0) = 12V, \quad \frac{dv(0)}{dt} = 48$$


- For $t > 0$, switch open, a series RLC network

$$\alpha = \frac{R}{2L} = 0.5, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2, \quad s_{1,2} = -0.5 \pm j1.936 \quad \text{Underdamped}$$

$$v(t) = v_{ss} + (A_1 \cos 1.936t + A_2 \sin 1.936t)e^{-0.5t}$$

$(C). R=1\Omega, V(0+)=12V, i(0+)=12A.$
 $\alpha = \frac{1\Omega}{2 \times 1H} = 0.5 \text{ rad/s}. \omega_0 = \frac{1}{\sqrt{1 \times 0.25}} = 2 \text{ rad/s}. \alpha < \omega_0.$
 Underdamped.
 $\Rightarrow S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -0.5 \pm j1.936.$
 $V(t) = e^{-0.5t} (B_1 \cos 1.936t + B_2 \sin 1.936t) + 24V.$
 From initial condition:
 $V(0+) = B_1 + 24 = 12 \Rightarrow B_1 = -12.$
 $i(0+) = C \frac{dV(t)}{dt} \Big|_{t=0+} = \frac{1}{4} (-0.5B_1 + 1.936B_2) = 12 \Rightarrow$
 $\begin{cases} B_1 = -12, \\ B_2 = 21.694. \end{cases} \Rightarrow V(t) = e^{-0.5t} (-12 \cos 1.936t + 21.694 \sin 1.936t) + 24V.$

parallel RLC Circuit

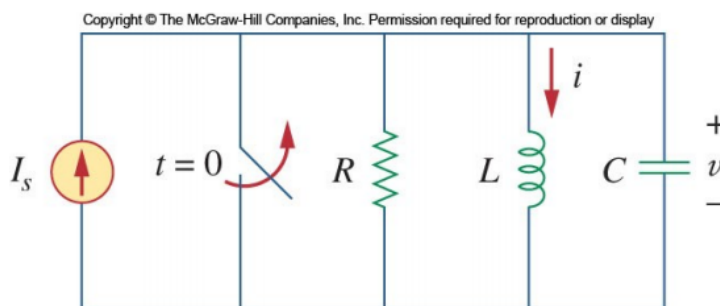

Apply KCL,

$$\frac{v}{R} + i + C \frac{dv}{dt} = I_s$$

But

$$v = L \frac{di}{dt}$$

So we get

$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC}$$

$$\frac{d^2 I}{dt^2} + \frac{1}{RC} \frac{dI}{dt} + \frac{I}{LC} = \frac{I_s}{LC} \quad (*)$$

Solution: $I(t) = \underbrace{I_t(t)}_{\text{transient response}} + \underbrace{I_{ss}(t)}_{\text{steady state response}}$

Statement: specifically, for step response, $I_t(t)$ is the same format as in natural response, $I_{ss} = I_s$, $v(t)$ is the solution to equation(*)


Case

$$\alpha = \frac{R}{2L}, \omega_0 = \sqrt{\frac{1}{LC}}$$

Case		$\alpha = \frac{R}{2L}, \omega_0 = \sqrt{\frac{1}{LC}}$	
1	overdamped	$\alpha > \omega \Leftrightarrow R > 2\sqrt{\frac{L}{C}}$	$I_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + I_s$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$
2	critically damped	$\alpha = \omega \Leftrightarrow R = 2\sqrt{\frac{L}{C}}$	$I_L(t) = (A_1 t + A_2) e^{s t} + I_s$ $s = -\alpha$
3	underdamped	$\alpha < \omega \Leftrightarrow R < 2\sqrt{\frac{L}{C}}$	$I_L(t) = e^{-\alpha t} [A_1 \cos \omega_d t + A_2 \sin \omega_d t] + I_s$ $\omega_0 = \sqrt{\omega_d^2 - \alpha^2}$

example

- Find $i(t)$ and $i_R(t)$ for $t > 0$.

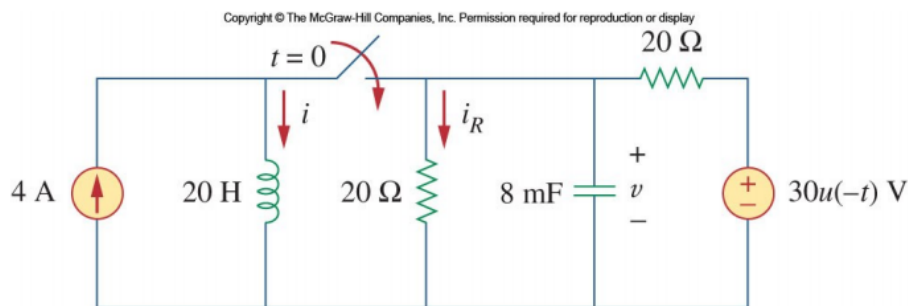

Initial values ($t < 0$): $i(0) = 4A$, $v(0) = \frac{20}{20+20} \times 30V = 15V = L \frac{di(0)}{dt}$

For $t > 0$, $\alpha = \frac{1}{2RC} = \frac{1}{2 \times 10 \times 8 \times 10^{-3}} = 6.25$, $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 8 \times 10^{-3}}} = 2.5$

$$s_{1,2} = -6.25 \mp 5.7282$$

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

General RLC Circuit

example

General RLC Circuits

- Find the complete response v for $t > 0$ in the circuit.

1. Initial conditions

$$v(0^+) = v(0^-) = 12V, i(0^+) = i(0^-) = 0$$

$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = \frac{-12/2}{0.5} = -12 V/s$$

2. Transient response

$$\text{KCL at node } a: i = \frac{v}{2} + 0.5 \frac{dv}{dt}$$

$$\text{KVL on left mesh: } 4i + 1 \frac{di}{dt} + v = 0$$

$$\Rightarrow \frac{d^2v}{dt^2} + 5 \frac{dv}{dt} + 6v = 0 \Rightarrow v_t(t) = A_1 e^{-2t} + A_2 e^{-3t} = 12e^{-2t} - 4e^{-3t}$$



3. Steady-state response

$$v_{ss}(t) = 4V$$

Lecture 6

4. Put together

35

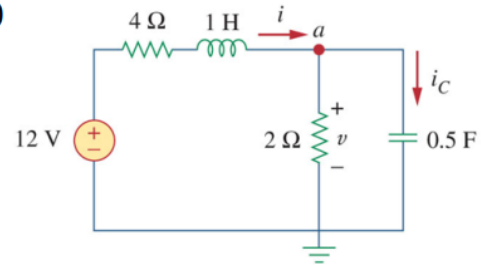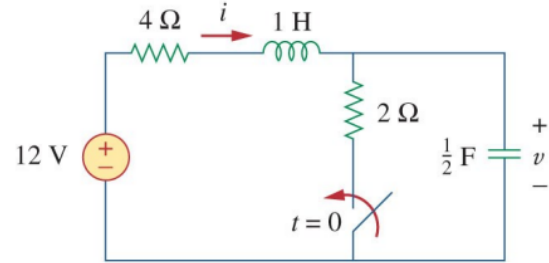

Summary

1. without excitation(Natural Response)自然响应

Case		$\frac{d^2y(t)}{dt^2} + 2\alpha \frac{dy(t)}{dt} + \omega_0^2 y(t) = 0$	
1	overdamped	$\alpha > \omega$	$y(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$
2	critically damped	$\alpha = \omega$	$y(t) = (A_1 t + A_2) e^{s t}$ $s = -\alpha$
3	underdamped	$\alpha < \omega$	$y(t) = e^{-\alpha t} [A_1 \cos \omega_d t + A_2 \sin \omega_d t]$ $\omega_0 = \sqrt{\omega_0^2 - \alpha^2}$

2. with any excitation

$$\frac{d^2y(t)}{dt^2} + 2\alpha \frac{dy(t)}{dt} + \omega_0^2 y(t) = f(t)$$

$$y(t) = y_h + y_p$$

y_h is the general solution to the corresponding homogeneous equation

y_p is a particular solution 特解

how to find y_p

1.

$$f(t)=e^{rt}P_m(t), P_m(t) \text{是关于} t \text{的} m \text{次多项式}, r \in \mathbb{R}$$

$$\begin{cases} r \neq s_{1,2}, & y_p=Qm(t)e^{rt} \\ r=s_1 \text{ or } s_2 (s_1 \neq s_2), & y_p=tQ_m(t)e^{rt} \\ r=s_1=s_2, & y_p=t^2Q_m(t)e^{rt} \end{cases}$$

2.

$$f(t)=e^{rt}(Mcos\omega t+Nsin\omega t), r,M,N,\omega \in \mathbb{R}, \omega \neq 0$$

$$\begin{cases} r\pm j\omega \neq s_{1,2}, & y_p=e^{rt}(B_1cos\omega t+B_2sin\omega t) \\ r\pm j\omega = s_{1,2}, & y_p=te^{rt}(B_1cos\omega t+B_2sin\omega t) \end{cases}$$

3.

\$\$

$$f(t)=f_{-1}(t)+f_{-2}(t)$$

$$y_{-p}=y_{-\{p-1\}}+y_{-\{p-2\}}$$

\$\$

$$f(t)=f_1(t)+f_2(t)y_p=y_{p_1}+y_{p_2}$$